

# 1 Design of Butterworth Lowpass Filter

## Butterworth Approximation

1. Define specification of the filter,  $H_0$ : DC Gain,  $H_c$ : Gain at cutoff frequency,  $H_s$  Gain at stopband edge frequency,  $\omega_c$ : Cutoff frequency (rad/s),  $\omega_s$ : Stopband frequency (rad/s). Also choose the optimization strategy: stopband edge frequency gain optimized or passband edge gain optimized.

2. Calculate normalized cutoff frequency  $\Omega_s$

$$\begin{aligned}\Omega_c &= 1 \\ \Omega_s &= \frac{\omega_s}{\omega_c}\end{aligned}$$

3. Calculate  $\beta = \beta_{max}$  on stopband edge frequency gain optimized or  $\beta = \beta_{min}$  on passband edge gain optimized.

$$\begin{aligned}\beta_{max} &= \sqrt{\left(\frac{H_0}{H_c}\right)^2 - 1} \\ \beta_{min} &= \sqrt{\frac{\left(\frac{H_0}{H_s}\right)^2 - 1}{\Omega_s^2}}\end{aligned}$$

4. Calculate the order of the filter  $N$  by rounding up  $n_{fmin}$  to the next integer:

$$n_{fmin} = \frac{\log\left(\frac{\frac{H_0^2}{H_s^2} - 1}{\frac{H_0^2}{H_c^2} - 1}\right)}{2 \log \Omega_s}$$

5. Calculate  $s_{k+}$ , the roots of the transfer function denominator polynomial equation:

$$s_{k+} = \sqrt[N]{\frac{1}{\beta}} e^{j\left(\frac{2k+1}{2N}\pi + \frac{\pi}{2}\right)} \quad k = 0, 1, \dots, N-1$$

**Example 1** Determine the transfer function of Butterworth lowpass filter of stopband edge frequency gain optimized,  $H_0 = 1$ ,  $H_c = 0.891$  ( = -1dB ) ,  $H_s = 0.00398$  ( = -48dB ) , Cutoff frequency = 125664 (=20kHz), Stopband edge frequency = 1108353 (=176.4kHz)

## 1. Perform Butterworth Approximation

$$\begin{aligned}
 \Omega_c &= 1 \\
 \Omega_s &= \frac{\omega_s}{\omega_c} = 8.82 \\
 n_{fmin} &= 2.85 \\
 N &= \text{Ceiling}(2.85) = 3 \\
 \beta_{max} &= 0.509 \\
 \text{angle of } s_k &= \frac{2k+1}{2N}\pi + \frac{\pi}{2} \\
 \text{magnitude of } s_k &= \beta^{\frac{-1}{N}} \\
 s_k &= \text{magnitude} \{ \cos(\text{angle}) + i \sin(\text{angle}) \} \\
 s_0 &= 1.25 \{ \cos(2.09) + i \sin(2.09) \} \\
 s_1 &= 1.25 \{ \cos(\pi) + i \sin(\pi) \} = -1.25 \\
 s_2 &= 1.25 \{ \cos(4.19) + i \sin(4.19) \}
 \end{aligned}$$

$$\text{Transfer function } H(s) = \frac{1}{(s - 1.25 \{ \cos(2.09) + i \sin(2.09) \})(s + 1.25)(s - 1.25 \{ \cos(4.19) + i \sin(4.19) \})}$$

## 2. Partial fraction decomposition

$$\begin{aligned}
 H(s) &= \frac{1}{(s - 1.25 \{ \cos(2.09) + i \sin(2.09) \})(s + 1.25)(s - 1.25 \{ \cos(4.19) + i \sin(4.19) \})} \\
 &= \frac{c_1}{s - 1.25 \{ \cos(2.09) + i \sin(2.09) \}} + \frac{c_2}{s + 1.25} + \frac{c_3}{s - 1.25 \{ \cos(4.19) + i \sin(4.19) \}} \\
 c_1 &= \frac{1}{(s + 1.25)(s - 1.25 \{ \cos(4.19) + i \sin(4.19) \})}, s = 1.25 \{ \cos(2.09) + i \sin(2.09) \} \\
 &= -0.6263 - 0.3616i \\
 c_2 &= \frac{1}{(s - 1.25 \{ \cos(2.09) + i \sin(2.09) \})(s - 1.25 \{ \cos(4.19) + i \sin(4.19) \})}, s = -1.25 \\
 &= 1.253 \\
 c_3 &= \frac{1}{(s - 1.25 \{ \cos(2.09) + i \sin(2.09) \})(s + 1.25)}, s = 1.25 \{ \cos(4.19) + i \sin(4.19) \} \\
 &= -0.6263 + 0.3616i \\
 \therefore H(s) &= \frac{-0.6263 - 0.3616i}{s + 0.6263 - 1.085i} + \frac{1.253}{s + 1.253} + \frac{-0.6263 + 0.3616i}{s + 0.6263 + 1.085i}
 \end{aligned}$$

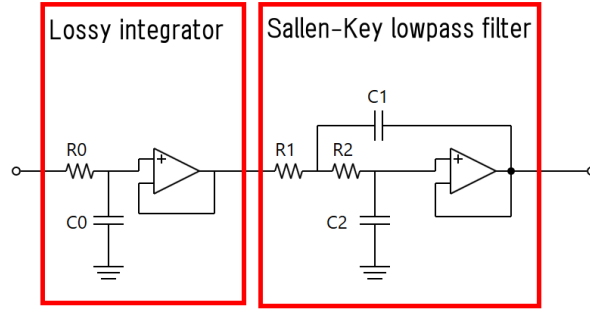


Figure 1

**3. Multiply conjugate complex 1st order rational polynomial to get 2nd order rational polynomial with real value coefficients**

$$\begin{aligned}
 H(s) &= \frac{-0.6263 - 0.3616i}{s + 0.6263 - 1.085i} + \frac{1.253}{s + 1.253} + \frac{-0.6263 + 0.3616i}{s + 0.6263 + 1.085i} \\
 &= \frac{1.253}{s + 1.253} + \frac{-0.6263 - 0.3616i}{(s + 0.6263 - 1.085i)(s + 0.6263 + 1.085i)} \\
 &= \frac{1.253}{s + 1.253} + \frac{0.523}{s^2 + 1.253s + 1.569}
 \end{aligned}$$

**4. Create lossy integrator from 1st order rational polynomial**

$$\begin{aligned}
 H_{s1} &= \frac{A}{s + a} \\
 \omega_c &= 20000 * 2 * \pi = 125663 \\
 R_{n0} &= 1 \\
 C_{n0} &= \frac{a}{\omega_c * R_0} \\
 R_0 &= R_{n0} * 10000 = 10(k\Omega) \quad (\text{frequency scaling}) \\
 C_0 &= \frac{C_0}{10000} = 996(\text{pF}) \quad (\text{frequency scaling})
 \end{aligned}$$

Bug: resulted circuit does not reflect A of the rational polynomial!

**5. Create Sallen-Key lowpass filter from 2nd order rational polynomial**

$$\begin{aligned}
H_{s2} &= \frac{A}{s^2 + as + b} \\
\omega_0 &= \sqrt{b} \\
\omega_c &= 20000 * 2 * \pi = 125663 \\
Q &= \frac{\omega_0}{a} \\
C_{n2} &= 1 \\
C_{n1} &= \sqrt{3} * Q * C_{n2} \\
R_{n1} &= \frac{1}{\omega_0 * Q * C_{n2}} \\
R_{n2} &= \frac{1}{\sqrt{3} * \omega_0 * C_{n2}} \\
C_1 &= \frac{C_{n1}}{\omega_c * 10000} = 1.38(\text{nF}) \quad (\text{frequency scaling}) \\
C_2 &= \frac{C_{n2}}{\omega_c * 10000} = 796(\text{nF}) \quad (\text{frequency scaling}) \\
R_1 &= R_{n1} * 10000 = 7.98(k\Omega) \quad (\text{frequency scaling}) \\
R_2 &= R_{n2} * 10000 = 4.61(k\Omega) \quad (\text{frequency scaling})
\end{aligned}$$

Bug: resulted circuit does not reflect A of the rational polynomial!